

6.004 Tutorial Problems

L06 – Boolean Algebra and Logic Synthesis

Note: A small subset of essential problems are marked with a red star (★). We especially encourage you to try these out before recitation.

A	B	C	F	G
0	0	0	1	1
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0

Strategy

Problem 1. ★

Consider the truth table on the right, which defines two functions F and G of three input variables (A, B, and C).

For each function, write it in **normal form**, then find a **minimal sum of products** (minimal SOP) expression.

①
$$\text{Normal form for } F(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC + A\bar{B}C$$

②
$$\bar{A}\bar{B}(\bar{C}+C) + (\bar{A}+A)B\bar{C} + (\bar{B}\bar{C})(\bar{A}+A)$$

③
$$\bar{A}\bar{B} + B\bar{C} + \bar{B}\bar{C}$$

Minimal sum of products for F(A,B,C) =

③
$$\bar{A}\bar{B}(\bar{C}+C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C$$

Normal form for G(A,B,C) =
$$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C$$

$$\bar{A}\bar{B}(\bar{C}+C) + \bar{A}C(\bar{B}+B) + (B\bar{C}+B)A\bar{C}$$

Minimal sum of products for G(A,B,C) =
$$\bar{A}\bar{B} + \bar{A}C + A\bar{C} = \bar{A}\bar{B} + \bar{C}$$

Problem 2. ★

Consider the 3-input Boolean function $G(A,B,C) = \bar{A} \cdot \bar{C} + A \cdot \bar{B} + \bar{B} \cdot \bar{C}$

1. How many 1's are there in the output column of G's 8-row truth table?

4

what = 1?
A=0 C=0
A=1 B=0
B=0 C=0

A	B	C	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

2. Give a minimal sum-of-products expression for G.

$$\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$$

$$\bar{A}\bar{C}(\bar{B} + B) + A\bar{B}(\bar{C} + C) = \bar{A}\bar{C} + A\bar{B}$$

3. There's good news and bad news: the bad news is that the stockroom only has G gates. The good news is that it has as many as you need. Using only combinational circuits built from G gates, one can implement (choose the best response):

- (A) Any Boolean function (G is functionally complete)
- (B) Only functions with 3 inputs or less
- (C) Only functions with the same truth table as G

is G functionally completely

$$G(A, B, 0)$$

⇒ NAND gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NAND

AB

4. Can a sum-of-products expression involving 3 input variables with greater than 4 product terms always be simplified to a sum-of-products expression using fewer product terms?

$2^3 = 8$

$$G(A, B, C)$$

+ + + +


$$\begin{aligned} G(A, B, 0) &= \bar{A} \cdot \bar{C} + A\bar{B} + \bar{B} \cdot \bar{C} \\ &= \bar{A} + A\bar{B} + \bar{B} \\ &= \bar{A} + \bar{B}(A+1) \\ &= \bar{A} + \bar{B} \\ &= \overline{A \cdot B} \end{aligned}$$

$$\bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

0 0 1 0 1 0

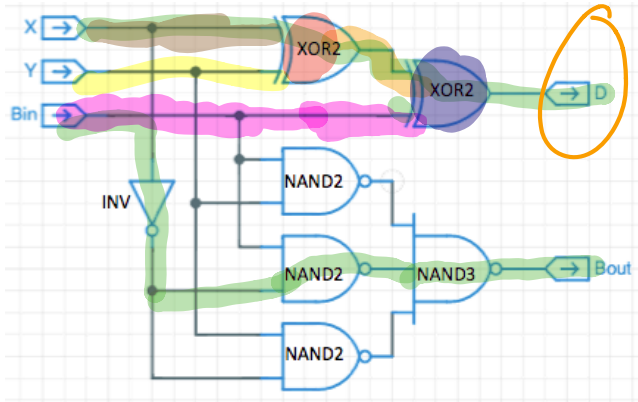Problem 3. ★

Consider the logic diagram shown below, which includes XOR2, NAND2, NAND3, and INV (inverter) gates.



Gate	t_{pd}
INV	1.0ns
NAND2	1.5ns
NAND3	1.8ns
XOR2	2.5ns

1. Using the t_{pd} information for the gate components shown in the table above, compute the t_{pd} for the circuit.

$X \rightarrow \text{XOR2} \rightarrow \text{XOR2} \rightarrow D$
 $2.5 + 2.5 = \underline{5 \text{ ns}}$

$\text{Bin} \rightarrow \text{inv} \rightarrow \text{NAND2} \rightarrow \text{NAND3} \rightarrow \text{Bout}$
 $1 + 1.5 + 1.8 = 4.3 \text{ ns}$

$t_{pd} = \underline{5} \text{ ns}$

2. Find minimal sum-of-products expressions for both outputs, **D** and **Bout**.

NOTE: The gates implement the following functions:

- $NAND2(a, b) = \overline{a \cdot b}$
- $NAND3(a, b, c) = \overline{a \cdot b \cdot c}$
- $XOR2(a, b) = \overline{a \cdot b} + \overline{\bar{a} \cdot \bar{b}}$

$XOR2(x, y) = x \cdot \bar{y} + \bar{x} \cdot y$
 Bin

$x\bar{y}\bar{\text{Bin}} + \bar{x}y\bar{\text{Bin}}$
 $+ xy\text{Bin} + \bar{x}\bar{y}\text{Bin}$

Minimal sum of products for **D(X,Y,Bin)** = _____

$(x \cdot \bar{y} + \bar{x} \cdot y) \bar{\text{Bin}} + (x \cdot \bar{y} + \bar{x} \cdot y) \text{Bin}$

$\overline{x \cdot \bar{y}} \cdot \overline{\bar{x} \cdot y}$
 $(\bar{x} + y) \cdot (x + \bar{y})$

Minimal sum of products for **Bout(X,Y,Bin)** = _____

$\bar{x} \cdot x + \bar{x} \bar{y} + xy + y \bar{y}$
 $= \underline{\underline{xy + \bar{x} \cdot \bar{y}}}$

Problem 4.

Simplify the following Boolean expressions by finding a *minimal sum-of-products expression* for each one:

1. $\overline{ac + b + c}$

2. $(a + b)c + \bar{c}a + b(\bar{a} + c)$

3. $\overline{a(b + c)}(b + a(b + c))$

4. $a(b + c(d + ef))$

Problem 5.

There are some Boolean expressions for which no assignment of values to variables can produce True (e.g., $a\bar{a}$). Those Boolean expressions are said to be *non-satisfiable*. Are the following Boolean expressions satisfiable? If the expression is satisfiable, give an assignment to variables that makes the expression evaluate to True. If the expression is non-satisfiable, prove it.

1. $(a + b)c + \bar{c}a + b(\bar{a} + c)$

2. $(x + y)(x + \bar{y})(z + \bar{y})(y + \bar{x})$

3. $(x + y + z)(x + y + \bar{z})(x + \bar{y} + z)(\bar{x} + y + z) \cdot$
 $(x + \bar{y} + \bar{z})(\bar{x} + y + \bar{z})(\bar{x} + \bar{y} + z)(\bar{x} + \bar{y} + \bar{z})$

4. $\overline{xyz + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} + \bar{x}yz + \bar{x}y\bar{z} + \bar{x}\bar{y}z}$

Problem 6.

(A) Simplify the following Boolean expressions by finding a minimal sum-of-products expression for each one. (*Note:* These expressions can be reduced into a minimal SOP by repeatedly applying the Boolean algebra properties we saw in lecture.)

1. $\overline{(a + b\bar{c})} \cdot d + c$

2. $a \cdot \overline{(b + c)}(c + a)$

(B) There are Boolean expressions for which no assignment of values to variables can produce True (e.g., $a\bar{a}$). These Boolean expressions are said to be *non-satisfiable*.


Are the following Boolean expressions satisfiable? If the expression is satisfiable, give an assignment to variables that makes the expression evaluate to True. If the expression is non-satisfiable, explain why.

1. $(\bar{x} + y\bar{z}) \cdot (\bar{y}x + z) \cdot (\bar{z}y + x)$

2. $(\bar{x} + y\bar{z}) \cdot (\bar{y}x + z) \cdot (\bar{z}y + x) + (\bar{x} + yz) \cdot (\bar{y}x + z) \cdot (\bar{z}y + x)$

Problem 7. Boolean Algebra and Combinational Logic (19 points, Spring 2020 Quiz 1) ★

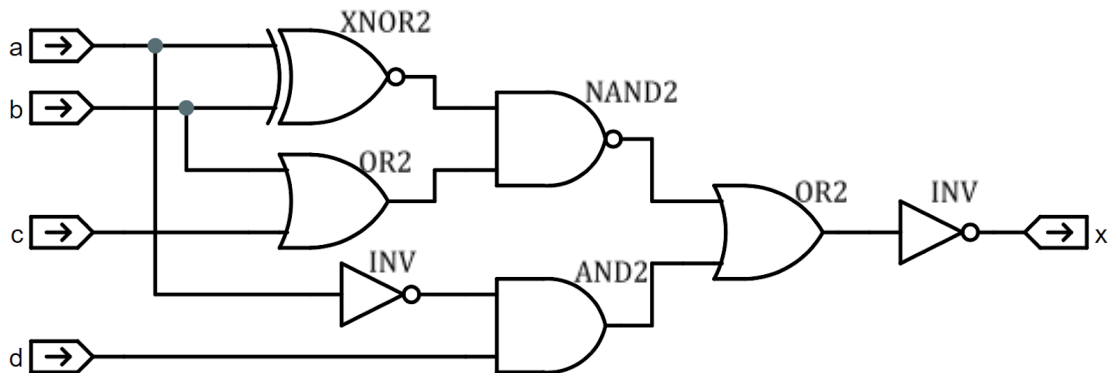(A) (3 points) Consider the logic diagram below, which includes XNOR2, OR2, NAND2, AND2, and INV. Using the t_{pd} information for the gate components shown in the table below, compute the t_{pd} for the circuit.




Gate	t_{pd}
XNOR2	7.0ns
OR2	5.5ns
NAND2	3.0ns
AND2	5.0ns
INV	2.0ns

t_{pd} (ns) = _____

(B) (6 points) Given the circuit shown below, construct the truth table for outputs **X** and **Y**.

a	b	c	X	Y
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

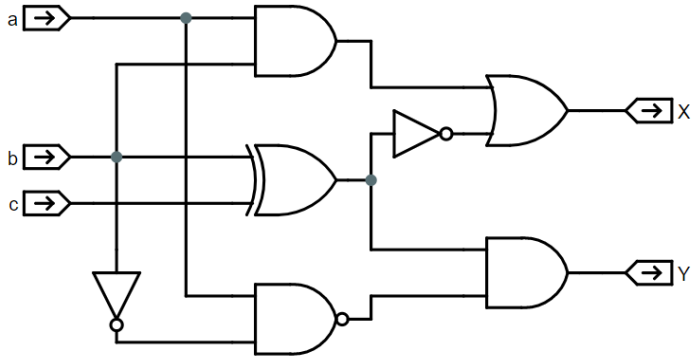

(C) (4 points) Find a minimal sum-of-products expression for output **X** of the circuit described by the truth table shown below.

a	b	c	d	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Minimal sum of products for **X** = _____

(D) (6 points) For each of the following expressions determine if it is satisfiable. If satisfiable, provide a minimal sum-of-products. Otherwise, show why it is not satisfiable.

1. $\overline{\overline{c}(a+b)(a+d)(ab\overline{c})}$

2. $(x+y)(x\overline{y}z + y\overline{z} + \overline{y})$